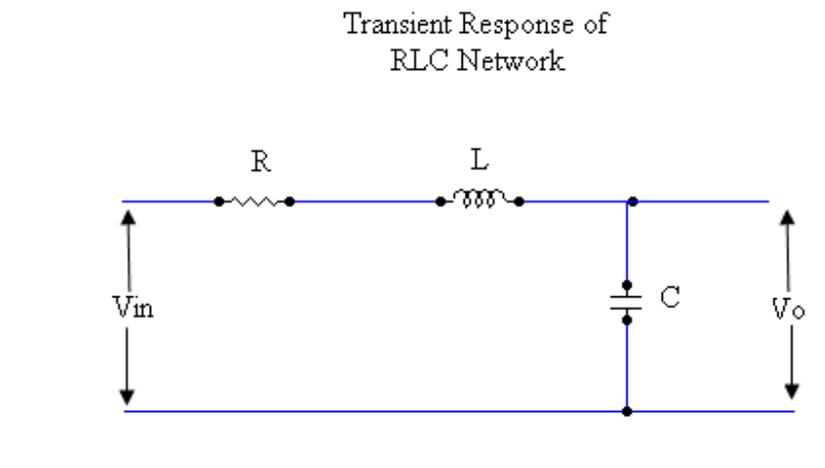


**Experiment No:3****Date:****Aim:**

To determine transient response of RLC network

**Apparatus:**

RLC network kit, patch cords, connecting wires etc.

**Diagram:****Theory:**

When system is given an excitation (I/p), there is a response (O/p). this response varies with time, and is called the time response Time response is divided in two parts:

**1. Transient Response:**

It is the part of response that goes to zero as a the time increases.

**2. Steady State Response:**

That part of the response that remain after the transients have died out.

**Order of The System:**

It is the highest power in the characteristics equation of the system.

**For example:**

$$S^2 + 2S + 1 = 0$$

Hence order of the system is two.

Consider the R, L, C network as shown in fig.

Using Kirchoffs voltage law,

$$V_i(s) = [R + LS + 1/CS] I(s)$$

And  $V_o(s) = I(s) / 1/CS$

Therefore transfer function.

$$\frac{V_o(s)}{V_i(s)} = \frac{1/LC}{S^2 + S R/L + 1/LC}$$

If we compare the equation with standard form of characteristics equation of second order system i.e.

$$S^2 + 2\rho \omega_n S + \omega_n^2 = 0$$

Then

$$\omega_n = \text{undamped natural frequency} = \sqrt{LC}$$

$$\rho = \text{damping ratio} = (R/2) * \sqrt{C/L}$$

and  $\omega_d = \text{Damped natural frequency} = \omega_n \sqrt{1 - \rho^2}$

The roots of the characteristic equation  $S^2 + 2\rho \omega_n S + \omega_n^2 = 0$  are

$$S_1, S_2 = -\rho \omega_n \pm \omega_n \sqrt{\rho^2 - 1}$$

### Case 1:

For  $0 < \rho < 1$ ;

The roots  $S_1$  &  $S_2$  are complex conjugate pair with -ve real part, and

$$V_o(t) = C(t) = 1 - (e^{-\rho \omega_n t} / \sqrt{1 - \rho^2}) * \sin(\omega_d t + \Phi)$$

where

$$\omega_d = \omega_n \sqrt{1 - \rho^2} \quad \& \quad \Phi = \cos^{-1} \rho$$

### Case II:

For  $\rho = 1$ ;

The roots  $S_1$  &  $S_2$  are real, -ve & equal and,

$$V_o(t) = 1 - e^{-\omega_n t} (1 + \omega_n t)$$

### Case III :-

For  $\rho > 1$ ;

The roots  $S_1$  &  $S_2$  are real, -ve & equal and,

$$V_o(t) = 1 + B e^{-S_1 t} + D e^{-S_2 t} \quad \text{where B, D ---- constants. and}$$

$$S_1, S_2 = -\rho \omega_n \pm \omega_n \sqrt{\rho^2 - 1}$$

**For**

**Case I :**

i.e.  $0 < \rho < 1$  is called as under damped.

**Case II**

i.e.  $\rho = 1$  is called as critically damped.

**Case III**

i.e.  $\rho > 1$  is called as over damped.

**Time Response Specification:**

**1. Delay time (td):**

It is the time required for the response to reach 50% of final value in first attempt.

**2. Rise time (tr):**

It is the time required for the response to rise from 10% to 90 % of the final value of the over damped system & 0 to 100% value of under damped system.

**3. Peak time (tp):**

It is the time required for the response to reach the peak of the response or the peak overshoot.

**4. Peak overshoot (MP):**

It indicates the normalized difference between the time response peak & steady state output.

It is defined as peak percent overshoot

$$\% M_p = \frac{C(t_p) - C(\omega)}{C(\omega)} * 100$$

Where  $C(t_p)$  is o/p at  $t = t_p$  and  $C(\omega)$  is steady state output.

**5. Settling time (ts):**

It is the time required for the response to reach & stay within a specific tolerance band of its final value.

**6. Steady State Error:**

It indicates the error between the actual o/p & desired o/p as  $t$  tends to infinity.

**Procedure:**

1. Make connection as shown in fig.
2. Adjust max. O/p voltage of repeated step I/p generator.
3. Make power on to the unit.
4. Connect CRO at the O/p & adjust CRO to get stable pattern on CRO.
5. Vary R by pot meter & for a given set of values of R,L,C. Study the transient response as observed on CRO.
6. Plot the same response on graph paper .
7. Study the pattern by using another set of L & C or by varying R.
8. Each time note the values of R,L,& C

**Observation Table:**

SR.NO.	R/ohm	L/mH	C/μF	$\rho = R/2\sqrt{C/L}$	$\omega_n = 1/\sqrt{LC}$	$\omega_d = \omega_n\sqrt{1-\rho^2}$
Set 1 $0 < \rho < 1$						
Set 2 P = 1						
Set 3 P = 1						

**Calculation:**

$$1. M_p = e^{-\pi \rho \sqrt{1-\rho^2}} * 100 \% =$$

$$2. tr = \frac{-\pi - \Phi}{\omega_d}$$

$$3. \text{Damping angle} = \Phi = \cos^{-1} \rho$$

$$4. t_p = \frac{\Pi}{\omega d}$$

$$5. t_s = \frac{4}{\rho \omega n} = \quad \text{for 2\% tolerance}$$

**Result :**

	MP calculated	MP observed
SET 1		
SET 1I		
SET 1II		

**Conclusion:**